

①

Name: Muhammad Istafa Malik.

Q.1

$(4F.B)_{16} - (29.A)_{16}$
With 2's C Method

4F 29
 ↙ ↘ ↙ ↘
 0100 1111 0010 1001

4F 0100 1111
 29 0010 1001

we will take 2's of 29

2's of 29 1101 0111

Now Add
 4F 0100 1111
 29 1101 0111 +

0 0100 110

Discard carry.

↓ ↓
 2 6

$(4F.B)_{16} - (29.A)_{16}$

$= (0010 \ 0110 \ . \ 0001)_2$
 ↓ ↓ ↓
 (2 6 . 1)₁₆

Now Fractional Part

B A
 ↓
 1011 1010

B 1011
 A 1010
 ———
 A 0101

Take 2's of

A 0110

Now Add

B 1011

2's of A 0110

0001
 discard carry

(2)

Q1 (b) $(-118)_{10} + (-32)_{10}$

	128	64	32	16	8	4	2	1
-	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	0

2's of 118 and 32

$$\begin{array}{r}
 11111111110001010 \\
 \text{Add } + \quad 11111111111000000 \\
 \hline
 \cancel{00000000000001101010}
 \end{array}$$

Taking 2's again for checking the decimal value

$$\begin{array}{r}
 0000000010010110 \\
 = 150
 \end{array}$$

So $1111111101101010 = (-150)_{10}$ in 2's

3

0 1000001 1011000

d)

01111111

X 00000101

① ① 01111111
 ① 00000000X
 01111111XX

1001111011

127

X 5

635

Now convert into Binary to Decimal

512	256	128	64	32	16	8	4	2	1
1	0	0	1	1	1	1		1	1

$$= 512 + 64 + 32 + 16 + 8 + 2 + 1$$

$$= 635$$

Verified

0100

④


Divisi

$$\begin{array}{r} 00001100 \overline{) 00100000} \\ \underline{00001100} \\ 00001100 \\ \underline{00001100} \\ 00000000 \end{array}$$

$$\begin{array}{r} 4 \overline{) 48} \\ \underline{48} \\ 0 \end{array}$$

X

5

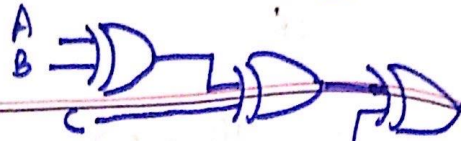

Q2

Expression

$$((A \oplus B) \oplus C) \oplus D$$

$$\text{Output 1} = ((1 \oplus 0) \oplus 0) \oplus 0$$

$$= (1 \oplus 0) \oplus 0$$

$$1 \oplus 0$$

$$1$$

$$\text{Output 2} : ((1 \oplus 1) \oplus 0) \oplus 1$$

$$= (0 \oplus 0) \oplus 1$$

$$(0) \oplus 1$$

$$1$$

$$\text{Output 3} : ((1 \oplus 0) \oplus 1) \oplus 0$$

$$(1 \oplus 1) \oplus 0$$

$$0 \oplus 0$$

$$0$$

Redraw Expression

$$((A \oplus B) \oplus C) \oplus D$$

$$((\bar{A}\bar{B} + \bar{A}B) \oplus C) \oplus D$$

$$((\bar{A}\bar{B} + \bar{A}B)\bar{C} + (\bar{A}\bar{B} + \bar{A}B)C) \oplus D$$

$$((\bar{A}\bar{B} + \bar{A}B)\bar{C} + (\bar{A}\bar{B} + \bar{A}B)C)\bar{D} + ((\bar{A}\bar{B} + \bar{A}B)\bar{C} + (\bar{A}\bar{B} + \bar{A}B)C)D$$

⑥

Q.3

Roll No = 19P-0033

Name = M. Istafa Malik.

My last Digit of Rollno is 3

A	B	C	D	Output
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

we will write
all the sop expressi
of these.

We will write this SOP form

$$\begin{aligned} &\bar{A}\bar{B}CD + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}BCD + A\bar{B}\bar{C}\bar{D} \\ &+ A\bar{B}CD + A\bar{B}\bar{C}\bar{D} + A\bar{B}CD + AB\bar{C}\bar{D} + AB\bar{C}D \\ &+ ABC\bar{D} + ABCD \end{aligned}$$

③

Q4

A	B	C	X	Y
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


Express for X in SOP

$$= \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

001
010
100
111

Kmap

AB \ C	0	1
00		1
01	1	
11		1
10	1	

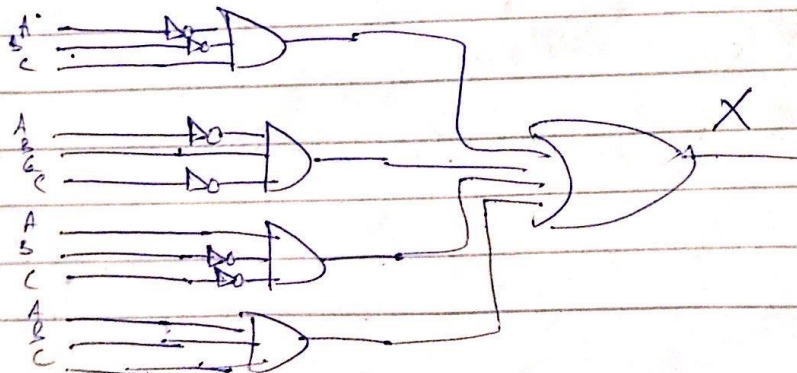


8


Expression for Y

$$\bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + ABC$$

001 010 011 111

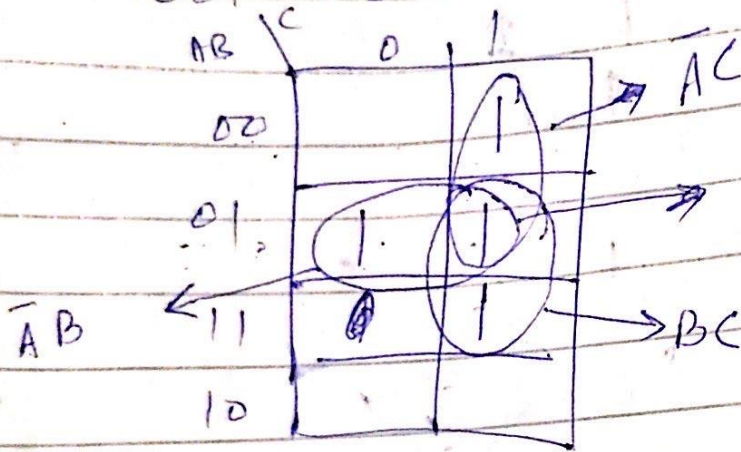

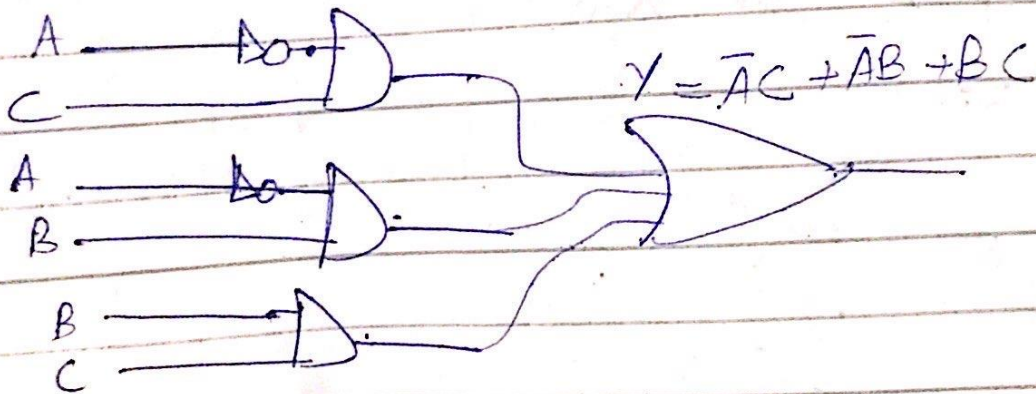Express after minimization. $\bar{A}C + \bar{A}B + BC$



9

Q6 For circuit 1

$$D_1 = \overline{AB} \cdot Z$$

$$D_1 = \overline{AB} + \overline{Z}$$

$$D_1 = AB + \overline{Z}$$

D		
D	Flop	Q
0	↑	0
1	↑	1

$D_1 = AB + \overline{Z}$	Z
0	0
1	1


[Assume Z is initially Low]

For circuit 2

$$D_2 = AB + \overline{Z}$$

[Note when A and B both 1, output will be 1 otherwise output will be 1 when Z is 0]

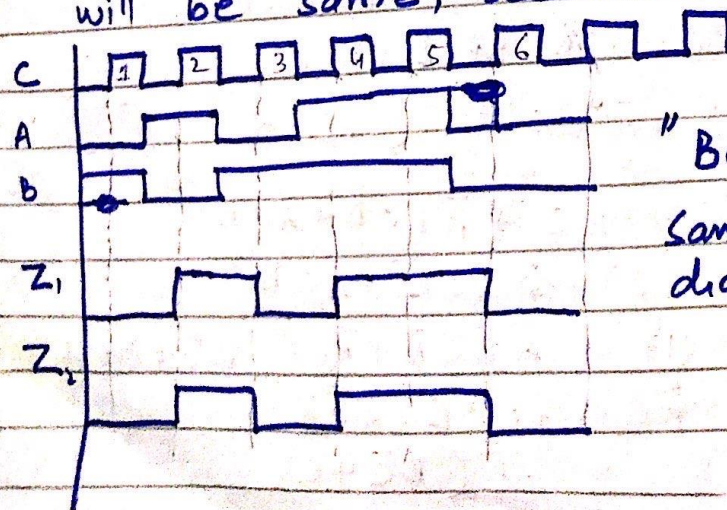Both have same input, so output Z will be same, because D flipflop.




"Both Z have same Time diagram."

(10)

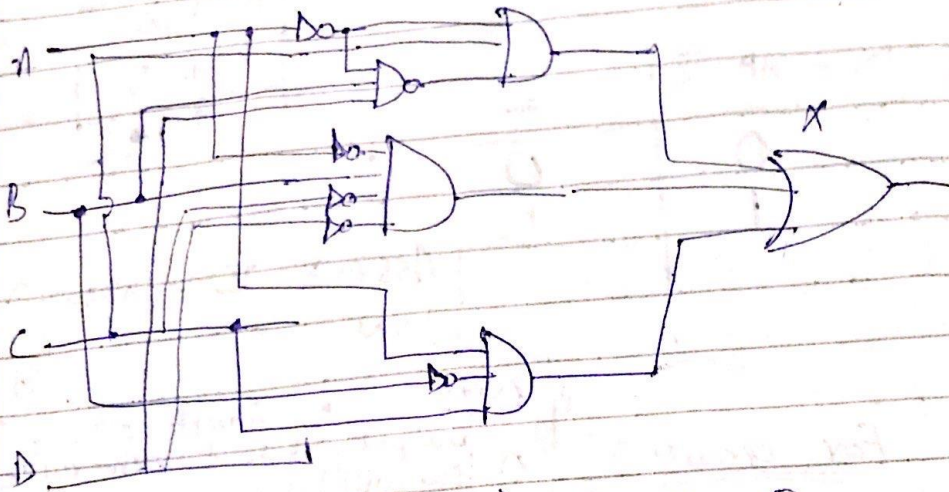Q7

$$\bar{A}C(\bar{A}BD) + \bar{A}B\bar{C}\bar{D} + \bar{A}BC$$



Simplify $\bar{A}C(\bar{A}BD) + \bar{A}B\bar{C}\bar{D} + \bar{A}BC$

$$\bar{A}C(\bar{A} + B + D) + \bar{A}B\bar{C}\bar{D} + \bar{A}BC$$

$$\bar{A}C(\bar{A} + B + D) + \bar{A}B\bar{C}\bar{D} + \bar{A}BC$$

$$A\bar{A}C + \bar{A}BC + \bar{A}C\bar{A} + \bar{A}B\bar{C}\bar{D} + \bar{A}BC$$

$$0 + \bar{A}BC + \bar{A}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}BC \quad \text{Rule } A\bar{A} = 0$$

$$\bar{A}BC + \bar{A}B\bar{C}\bar{D} + \bar{A}C\bar{D} + \bar{A}BC$$

$$\bar{A}BC + \bar{A}BC + \bar{A}B\bar{C}\bar{D} + \bar{A}C\bar{D}$$

$$\bar{B}C(\bar{A} + A) + \bar{A}B\bar{C}\bar{D} + \bar{A}C\bar{D}$$


$$\bar{B}C(1) + \bar{A}B\bar{C}\bar{D} + \bar{A}C\bar{D} \quad \text{Rule } A + \bar{A} = 1$$

$$\bar{B}C + \bar{A}B\bar{C}\bar{D} + \bar{A}C\bar{D}$$

$$\bar{B}C + \bar{A}\bar{D}(B\bar{C} + C)$$


①
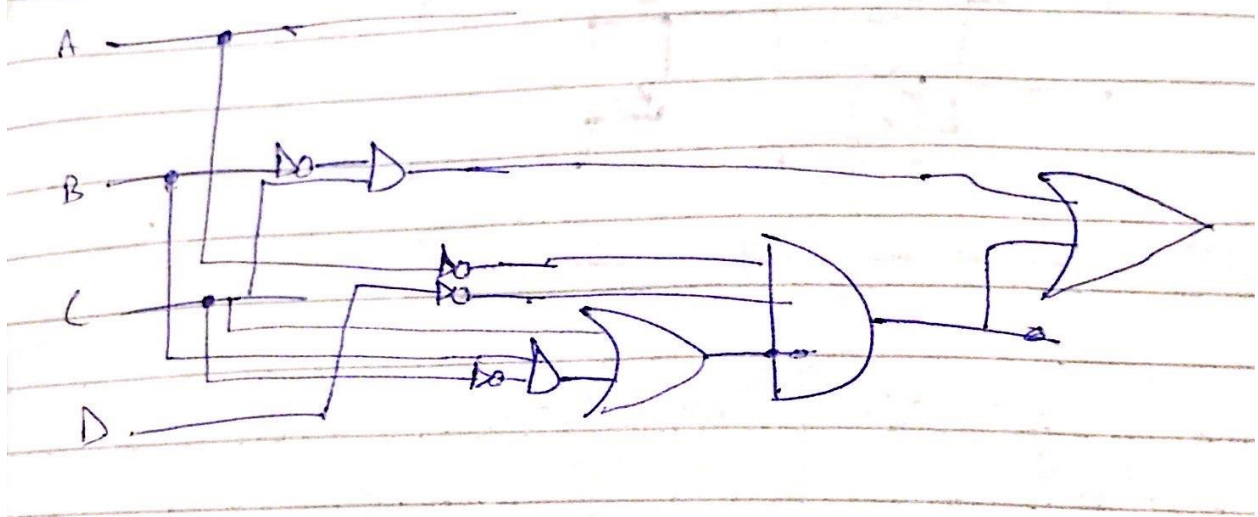
$$\overline{B}C + \overline{A}D (B\overline{C} + C)$$



⑫

Q9

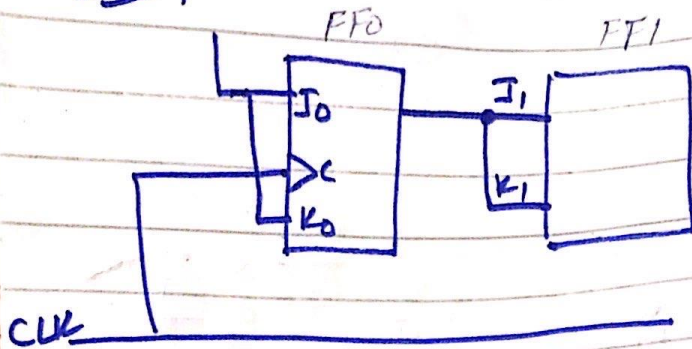


The operation of this synchronous counter is as follows. First, assume that the counter is initially in the binary 0 state; that is, both flip flops are reset. When the positive edge of the first clock pulse is applied, FF0 will toggle and Q₀ will be therefore go high. What happens to FF1 at the rising edge of CLK? To find

look at the input conditions of FF1. Inputs J₁ and K₁ are both low because Q₀ to which they are connected has not yet gone high. Remember there is a propagation delay.

Q5:

Q5

D_1	D_0	D_2	D_L	A_2
s_1, s_0	s_1, s_0	s_1, s_0	s_1, s_0	s_1, s_0
01	00	11	01	10

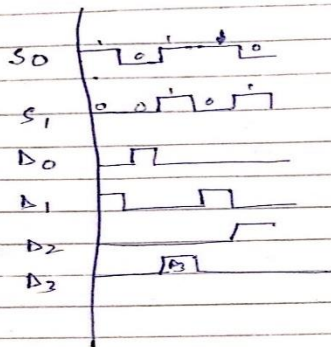

s_1	s_0	
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3